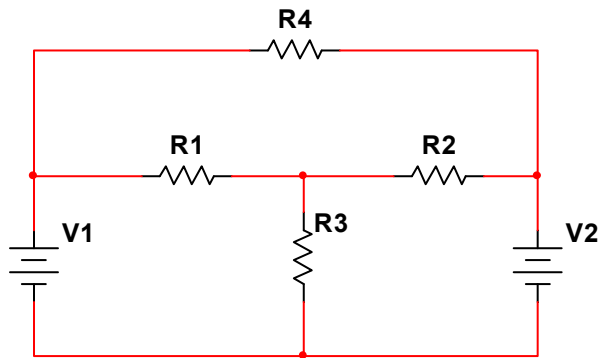


**FLORIDA INTERNATIONAL UNIVERSITY**  
**COLLEGE OF ENGINEERING AND COMPUTING**  
**DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING**

*EEL 3110L-CIRCUITS LAB*

**SECOND ACTIVITY:** Introduction to Kirchhoff's Voltage Law, Kirchhoff's Current Law, Superposition, as well as do the computer simulations before or after the lab (it's recommended that you do them before).

1-Set up the following circuit.



- a)  $R_1 \geq 1\text{k}\Omega$
- b)  $R_2 \geq R_1$
- c)  $2.2\text{ k}\Omega \leq R_3 \leq 10\text{k}\Omega$
- d)  $470\Omega \leq R_4 \leq 100\text{ k}\Omega$
- e)  $2\text{ volts} \leq V_1 \leq 7\text{ volts}$
- f)  $1\text{ volt} \leq V_2 \leq 20\text{ volts}$

Verify Kirchhoff's Voltage Law and Kirchhoff's Current Law.

Also find the power absorbed by  $R_3$ .

Measure and tabulate all currents and voltages.

Briefly explain and comment your results.

---

**2-** Using the same circuit as above, verify the Superposition Theorem.

Measure and tabulate all currents and voltages.

Briefly explain and comment your results.

---

Write a brief summary of today activities. Remember to keep your records and own comments in your lab notebook.