


**FLORIDA INTERNATIONAL UNIVERSITY**  
**COLLEGE OF ENGINEERING AND COMPUTING**  
**DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING**

*EEL 3110L-CIRCUITS LAB*

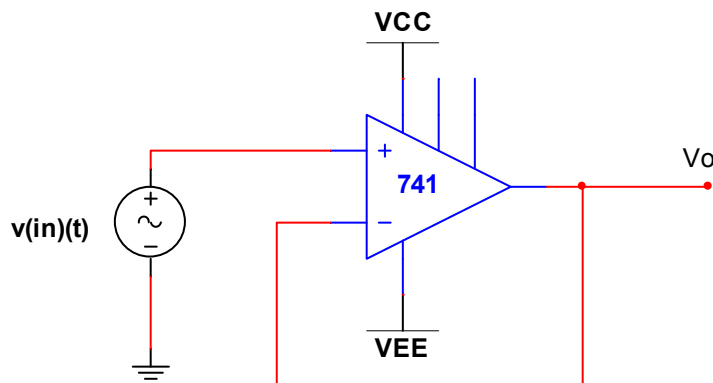**FIFTH ACTIVITY: Op-Amps II**

Please do the computer simulations before or after the lab (it's recommended that you do them before).

1- Set up the following circuits with the Op-Amp properly biased (Not shown).



$$v_{in}(t) = V_m \sin(\omega t)$$

$$V_m \geq 1 \text{ volt}$$


Measure and Graph  $v_o(t)$  for each  $\omega$ :

$$\omega = 205 \text{ rad/s}, 6283 \text{ rad/s}, 125663 \text{ rad/s}.$$

Briefly explain and comment your results

-----

2- Set up the following circuit.

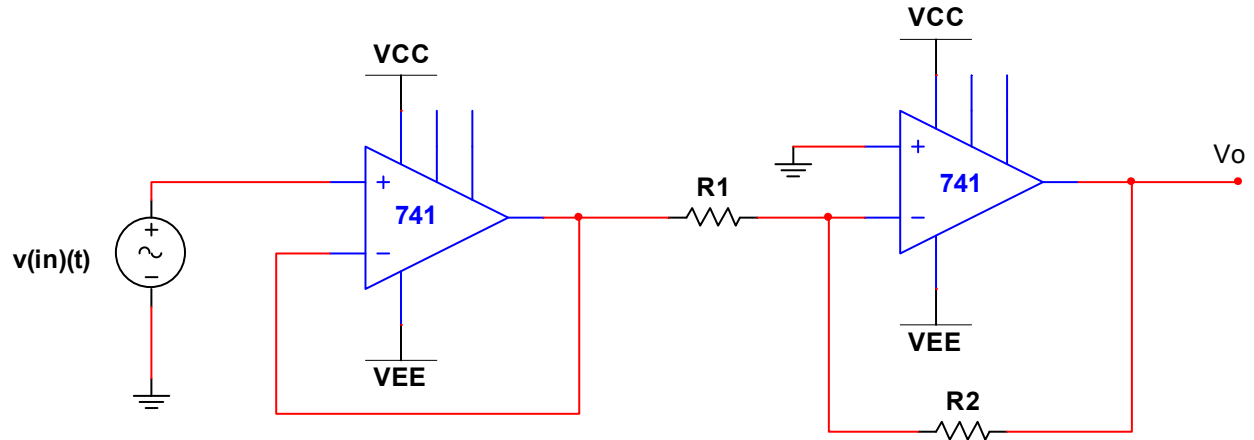

\*\*\*note:  $V_{cc}$  and  $V_{ee}$  are not shown in the drawing. Use the same value of  $V_{cc}$  and  $V_{ee}$  as before.

$$v_{in}(t) = V_m \sin(\omega t)$$

$$V_m \geq 1 \text{ V}$$

$$\omega \geq 6283 \text{ rad/s}$$

Measure and Graph  $V_{in}(t)$  and  $V_o$  (compare it in the same window) for the given conditions.

Take note of the gain:  $(A_v = \frac{v_o}{v_{in}})$

$$R1 = R2$$

$$R1 > R2$$


$$R1 < R2$$

$$R1 = 100\Omega, R2 = M\Omega,$$

Briefly explain and comment your results.

---

3- Set up the following circuit.

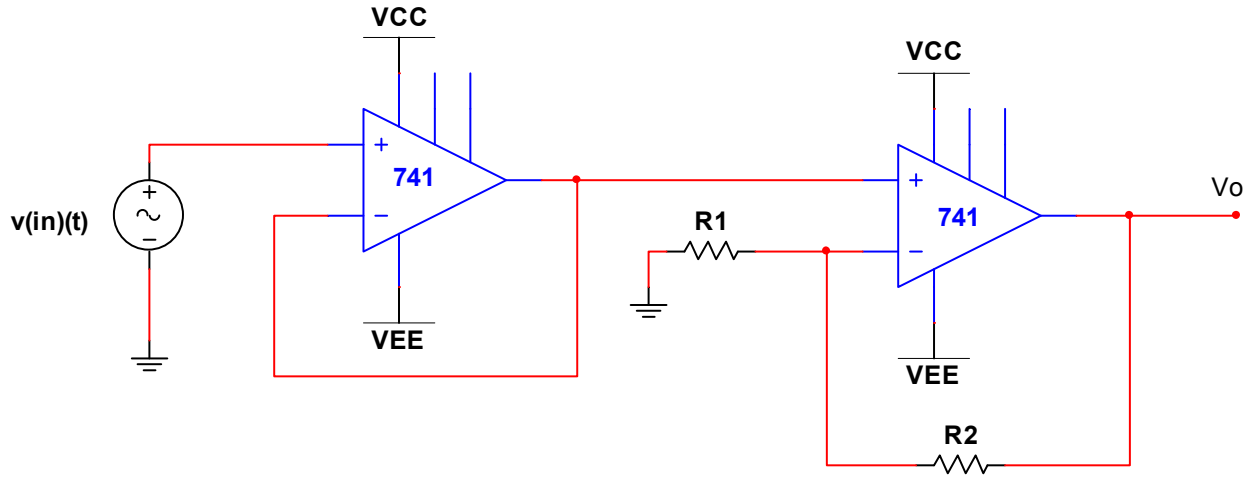

\*\*\*note:  $V_{cc}$  and  $V_{ee}$  are not shown in the drawing. Use the same value of  $V_{cc}$  and  $V_{ee}$  as before.

$$v_{in}(t) = V_m \sin(\omega t)$$

$$V_m \geq 1 \text{ V}$$

$$\omega \geq 6283 \text{ rad/s}$$

Measure and Graph  $V_{in}(t)$  and  $V_o$  (compare it in the same window) for the given conditions.

Take note of the gain:  $(A_v = \frac{v_o}{v_{in}})$

$$R1 = R2$$

$$R1 > R2$$

$$R1 < R2$$

$$R1 = 100\Omega, R2 = M\Omega,$$

Briefly explain and comment your results.

---

Write a brief summary of today activities. Remember to keep your records and own comments in your lab notebook.