


FLORIDA INTERNATIONAL UNIVERSITY
COLLEGE OF ENGINEERING AND COMPUTING
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

EEL 3110L-CIRCUITS LAB


SEVENTH ACTIVITY: Transient Response of R-C circuit and Intro to Transformer

Please do the computer simulations before or after the lab (it's recommended that you do them before).

1- Set up the following circuit.

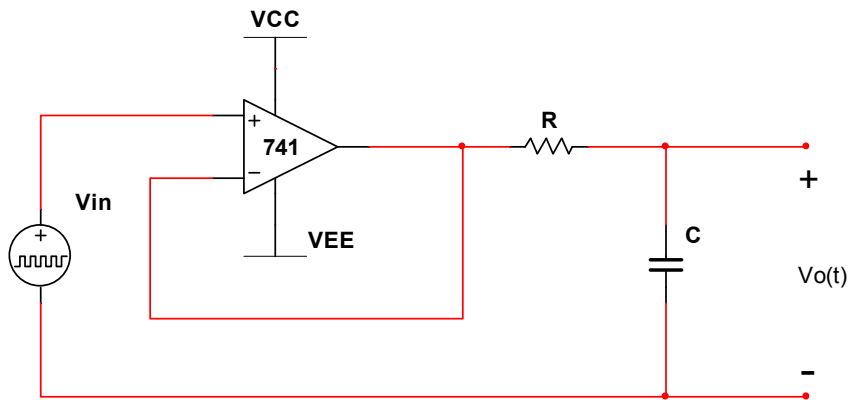

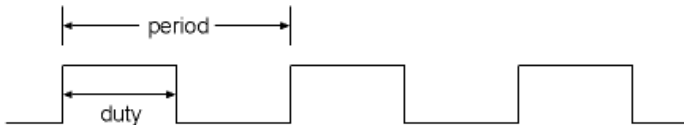$v_{in}(t)$: Square Wave with Duty Cycle = 0.5 where Duty Cycle = $\frac{\text{duty}}{\text{period}}$



Set frequency for the following conditions knowing that $f = \frac{1}{T}$ and $\tau = RC$


- a) $T = \tau$
- b) $T = 100\tau$
- c) $T = \frac{1}{100} \tau$
- d) $T = \frac{1}{2} \tau$
- e) $T = 2\tau$

Graph $v_o(t)$ for each conditions above

Briefly explain and comment your results

2- Introduction to Transformer

a) Set up the following circuit

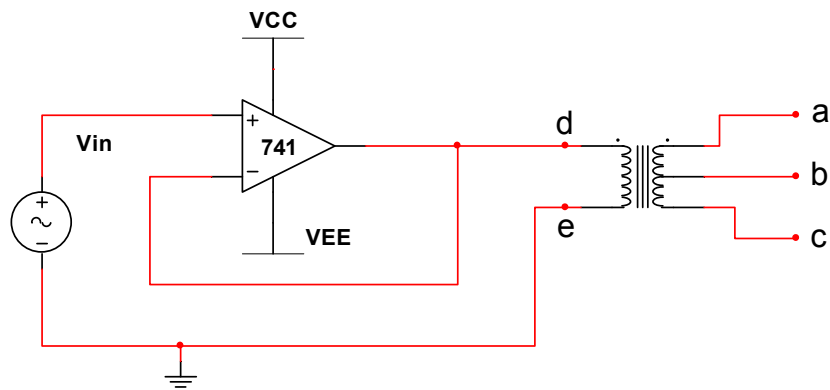

$v_{in}(t) = V_m \sin(\omega t)$, $V_m \geq 15\text{V}$, where $\omega = 377 \text{ rad/s}$


Measure the amplitude of the V_{de} , V_{ab} , V_{bc} , V_{ac} , calculate their RMS values.

Also, find the turn ratio of:

- i. (d-e) : (a-b)
- ii. (d-e) : (b-c)
- iii. (d-e) : (a-c)

Briefly explain and comment your results

b) Set up the following circuit

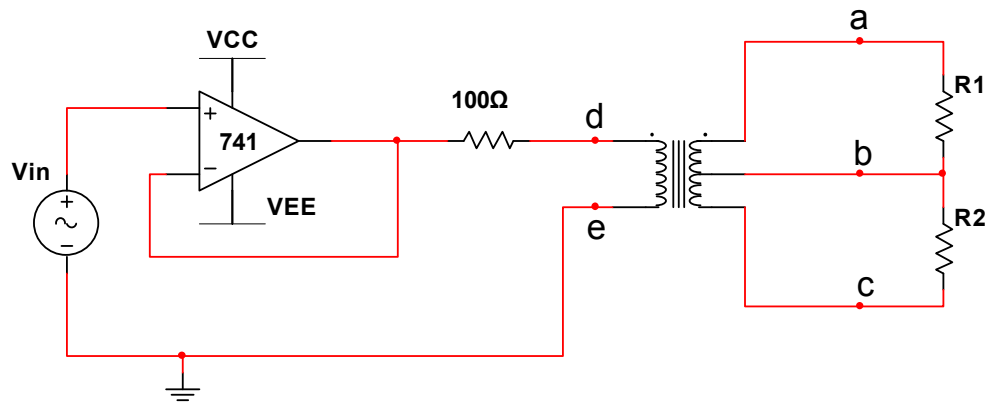

$$470\Omega \leq R_1 = R_2 \leq 2.2\text{k}\Omega$$

Repeat the measurements above

Briefly explain and comment your results

Write a brief summary of today activities. Remember to keep your records and own comments in your lab notebook.